

9. In three phase power measurement using two wattmeters if one wattmeter reads zero what will be the power factor of the circuit?
10. Define coefficient of coupling.

PART B — (5 × 16 = 80 marks)

11. (a) (i) State and explain Kirchoff's Laws. (8)
- (ii) Two resistors are connected in parallel and a voltage of 200 V is applied to its terminals. The total current taken is 25 A and the power dissipated in one of the resistors is 1500 W. What is the resistance of each resistor? (8)

Or

- (b) (i) A circuit has 'n' resistance connected in parallel. Derive the relationship between the current through each resistor and the circuit current. (8)
- (ii) Two resistors $R_1 = 2500 \Omega$ and $R_2 = 4500 \Omega$ are joined in series and connected to a 100 V supply. The voltage drop across R_1 and R_2 are measured successively by a voltmeter having a resistance of $50,000 \Omega$. Find the sum of the two readings. (8)

12. (a) (i) Derive an expression for transient current of an RL series circuit subjected to a step increase in voltage at $t = 0$. Define time constant and derive equation for time constant for this circuit. (8)
- (ii) A direct voltage applied to a coil of $L = 1 \text{ H}$ and $R = 10 \Omega$ is suddenly changed from V_1 to V_2 . Calculate the current for $t = 0.05$ secs, if
- (1) $V_1 = 100 \text{ V}$ and $V_2 = 200 \text{ V}$;
- (2) $V_1 = 200 \text{ V}$ and $V_2 = 100 \text{ V}$. (8)

Or

- (b) (i) A circuit of resistance 20Ω and inductance 0.2 H in series has a direct voltage of 250 V suddenly applied to it. Find the voltage drop across the inductor at the instant of switching and at 0.01 secs later. (8)
- (ii) Express the impedance $z(s)$ of the parallel combination of $L = 4 \text{ H}$ and $C = 1 \mu\text{F}$. At what frequencies the impedance becomes infinite? (8)

13. (a) (i) A resistor of $100\ \Omega$ is connected in series with a $50\ \mu F$ capacitor to a supply at $200\ V$, $50\ Hz$. Find the circuit current and power factor. Draw the phasor diagram. (8)
- (ii) Obtain the power and power factor of the circuit shown in fig 13 (a) (ii). (8)

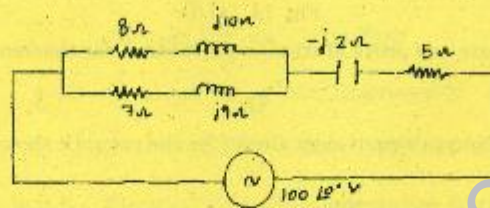


Fig. 13 (a) (ii)

Or

- (b) (i) Obtain the expression for resonant frequency for the circuit shown in fig 13.(b) (i). (8)

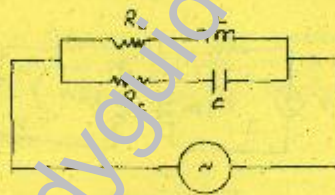


Fig. 13. (b) (i)

- (ii) A coil having a resistance of $5\ \Omega$ and an inductance of $0.1\ H$ is connected in series with a $50\ \mu F$ Capacitor and a supply voltage of $200\ V$ is applied across the circuit. What will be frequency of supply voltage at which current is maximum? Calculate the current and voltage magnification at resonance? (8)

14. (a) (i) Calculate V_A and V_B in the circuit shown in fig. 14 (a) (i), using Nodal Analysis. (8)

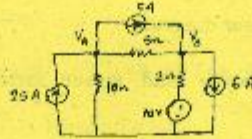


Fig. 14. (a) (i)

- (ii) State and prove Maximum Power transfer theorem for A.C Circuits. (8)

Or

- (b) Obtain Norton's equivalent circuit for the network shown in fig. 14. (b). (16)

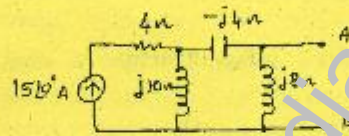


Fig. 14 (b)

15. (a) (i) In the coupled circuit shown in fig. 15.(a)(i), find V_2 for which $I_1 = 0$. (8)



Fig. 15 (a) (i)

- (ii) What are symmetrical components. Derive equation for symmetrical components in terms of three phase voltage. (8)

Or

- (b) Determine the line currents and their phase angles in an unbalanced star connected load supplied from a symmetrical three phase 440 V supply. The branch impedances of load are $Z_U = 5\angle30^\circ \Omega$, $Z_V = 5\angle30^\circ \Omega$ and $Z_W = 5\angle30^\circ \Omega$; The phase sequence is RYB. (16)